

$$V_{nc} := \frac{V_c Z_p}{R + Z_p}$$

[STUDENT > # Find Vnb by simple voltage divider

[STUDENT > Vnb:=Vb*(R/2)/(R/2 + Zc);

$$V_{nb} := \frac{1}{2} \frac{V_b R}{\frac{1}{2} R + Z_c}$$

[STUDENT > # Vn is sum of Vna, Vnb, Vnc:

[STUDENT > Vn:=Vna+Vnb+Vnc;

$$V_n := \frac{V_a Z_p}{R + Z_p} + \frac{1}{2} \frac{V_b R}{\frac{1}{2} R + Z_c} + \frac{V_c Z_p}{R + Z_p}$$

[STUDENT > # Compute values of Zc and Zp which will be used in Vn

[STUDENT > Zc:=1/(I*w*C);

$$Z_c := -\frac{I}{w C}$$

[STUDENT > Zp:=Zc*R/(Zc+R);

$$Z_p := -\frac{I R}{w C \left(-\frac{I}{w C} + R \right)}$$

[STUDENT > # Display Vn with new values Zc and Zp substituted

[STUDENT > Vn;

$$\begin{aligned} & -\frac{I V_a R}{w C \left(-\frac{I}{w C} + R \right) \left(R - \frac{I R}{w C \left(-\frac{I}{w C} + R \right)} \right)} + \frac{1}{2} \frac{V_b R}{\frac{1}{2} R - \frac{I}{w C}} \\ & -\frac{I V_c R}{w C \left(-\frac{I}{w C} + R \right) \left(R - \frac{I R}{w C \left(-\frac{I}{w C} + R \right)} \right)} \end{aligned}$$

[STUDENT >

[STUDENT >

[STUDENT >

[STUDENT > # Simplify

[STUDENT > Vn:=simplify(Vn);

$$V_n := \frac{-I V_a + V_b R w C - I V_c}{-2 I + R w C}$$

[STUDENT > # THE ABOVE EXPRESSION IS ENOUGH TO ANSWER THE QUESTION

[STUDENT > # ASSUME R*w*C <<1. => Denominator ~ -2 *I

```

[ STUDENT > # Numerator is  $-I(V_a + V_c) + V_b * R * w * C$ 
[ STUDENT > # When we divide numerator by  $-2*I$  we get
[ STUDENT > #  $V_n \sim 0.5 * [(V_a + V_c) + I * V_b * R * w * C]$ 
[ STUDENT > # Now we will simply assume  $V_b = 1$  ANGLE 0
[ STUDENT > # This covers both scenarios
[ STUDENT > #   ABC rotation:  $\{V_b=1, V_c=1/A, V_a=1/A^2\}$ ;
[ STUDENT > #   ACB rotation:  $\{V_b=1, V_a=1/A, V_c=1/A^2\}$ ;
[ STUDENT >
[ STUDENT > # Since  $V_a$  and  $V_c$  appear symmetrically, we will get the
[         same solution  $V_n$ 
[ STUDENT > #   regardless of which orientation one we choose
[ STUDENT >
[ STUDENT > # To find out whether  $V_n$  is closer to  $V_a$  or  $V_c$  we need
[         only look at the imaginary part of
[ STUDENT > #  $V_n \sim 0.5 * [(V_a + V_c) + I * V_b * R * w * C]$ 
[ STUDENT > # given that we assumed  $\text{angle}(V_b)=0$ , we know
[ STUDENT > #    $V_a+V_c$  is real
[ STUDENT > #    $V_b$  is real and positive
[ STUDENT >
[ STUDENT > #   So we see imaginary part is
[ STUDENT > #    $\text{Im}(V_b) = I * V_b * R * w * C$ 
[ STUDENT >
[ STUDENT > #   Since  $V_b$  is positive, the imaginary part of  $V_n$  is
[         positive
[ STUDENT > #   If we choose ABC rotation,  $V_n$  is closer to  $V_a$  and light
[         attached to A will be dimmer
[ STUDENT > #   If we choose ACB rotation,  $V_n$  is closer to  $V_c$  and light
[         attached to C will be dimmer
[ STUDENT >

```