$$V_{\rm S} = 13.8 \, kV$$
  
 $V_{\rm R} = 13.8 \, kV$   
 $\delta = 5^{\circ}$   
 $X_{\rm L} = 0.1 \, \Omega$ 

Base case values of  ${\tt P}$  and  ${\tt Q}$ 

$$P := \frac{V_{S} \cdot V_{R} \cdot \sin(\delta)}{X_{L}} \qquad P = 166 MW$$
$$Q := \frac{V_{S} \cdot V_{R} \cdot \cos(\delta) - V_{R}^{2}}{X_{L}} \qquad Q = -7 Mvar$$

Values of P and Q with 5% increase in sending end voltage, with power angle constant

$$V_{S1} \coloneqq 1.05 \cdot 13.8 \, kV$$

$$P_{1} \coloneqq \frac{V_{S1} \cdot V_{R} \cdot \sin(\delta)}{X_{L}}$$

$$P_{1} = 174 \, MW$$
Note that both P and Q change, but Q changes much more than P for the change in sending end voltage
$$Q_{1} \coloneqq \frac{V_{S1} \cdot V_{R} \cdot \cos(\delta) - V_{R}^{2}}{X_{L}}$$

$$Q_{1} \equiv \frac{W_{S1} \cdot V_{R} \cdot \cos(\delta) - V_{R}^{2}}{X_{L}}$$

$$Q_{1} \equiv 88 \, Mvar$$

Values of P and Q with 5% increase in power angle, with sending end voltage constant

$$\delta_{2} \coloneqq 1.05 \cdot 5^{\circ}$$

$$P_{2} \coloneqq \frac{V_{S} \cdot V_{R} \cdot \sin(\delta_{2})}{X_{L}}$$

$$P_{2} \equiv \frac{V_{S} \cdot V_{R} \cdot \cos(\delta_{2}) - V_{R}^{2}}{X_{L}}$$

$$Q_{2} \coloneqq \frac{V_{S} \cdot V_{R} \cdot \cos(\delta_{2}) - V_{R}^{2}}{X_{L}}$$

$$Q_{2} \equiv -8 Mvar$$

Note that both P and Q change, but P changes much more than Q for the change in power angle