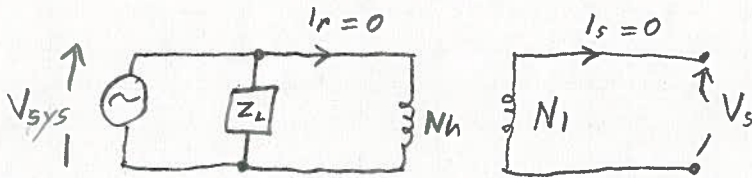


Note: Analysis uses an ideal transformer model which doesn't exist in the real world. It is only meant to illustrate fundamental concepts!



VT connection with open circuit

V_{sys} = System voltage

V_s = secondary voltage


N_h = higher # of winding turns

N_l = lower # of winding turns

Z_L = load impedance

$V_s = V_{sys} * \left(\frac{N_l}{N_h} \right)$ or V_s is V_{sys} adjusted down by the VT turns ratio

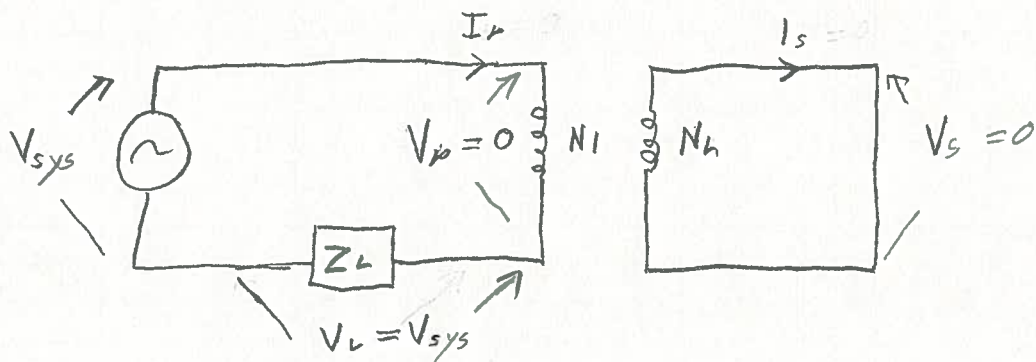$V_L = \text{load voltage}$, $V_p = \text{Ct primary voltage}$




Ct Connected normally

$$I_p = V_p / Z_L$$

$$I_s = I_p * \frac{N_1}{N_2}$$

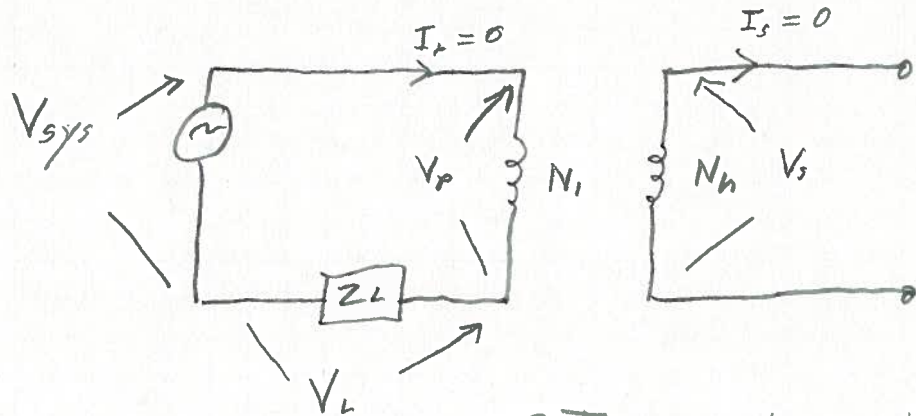or $I_s = I_p$ adjusted
down by the Ct
turns ratio



CT connection with open circuit secondary

$$V_L = I_p * Z_L = 0$$

$$V_L + V_p = V_{sys}$$

$$V_p = V_{sys}$$

$$V_s = V_{sys} * \frac{N_h}{N_1}$$

OR $V_s =$ System voltage stepped up by the CT turns ratio.