



Two each single phase 480V primary 120V secondary xfrms connected in boosting autotransformer configuration.  
 Xfrm: 50KVA, 5%Z Nameplate  
 Solve for fault on secondary.