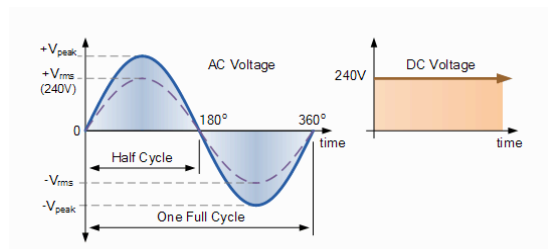


Source Voltage  $U_{rms} := 400 \text{ V}$

Source Voltage  $f_{in} := 50 \text{ Hz}$



Peak voltage for in the DC bus section  $U_{peak} := U_{rms} \cdot \sqrt{2}$   $U_{peak} = 565,6854 \text{ V}$

$$U_{av} := \frac{U_{peak}}{1,11} \quad U_{av} = 509,6265 \text{ V}$$

The winding of a motor can be simplified to a RL circuit

The impedance of the circuit will be:

frequency of varied voltage  $U_v := 400 \text{ V}$

frequency of varied Hz  $f_v := 50 \text{ Hz}$

Resistance  $R_{winding} := 5 \text{ ohm}$

Inductance  $L_1 := \frac{R_{winding} \cdot \sqrt{3}}{2 \cdot \pi \cdot f_v}$   $L_1 = 27,5664 \text{ mH}$

Inductive reactance.  $X_1 := 2 \cdot \pi \cdot f_v \cdot L_1$   $X_1 = 8,6603 \Omega$

capacitance  $C_1 := 0,001 \text{ farad}$

Inductive reactance.  $X_c := \frac{1}{2 \cdot \pi \cdot f_v \cdot C_1}$   $X_c = 3,1831 \Omega$

impedence  $Z_1 := \sqrt{R_{winding}^2 + (X_1 + X_c)^2}$   $Z_1 = 12,8555 \Omega$

If the current and frequency maintain the same ratio below the motor value, the current also remains constant. If the current is constant, the torque is also constant.

Current  $I_x := \frac{U_v}{\sqrt{R_{winding}^2 + (2 \cdot \pi \cdot f_v \cdot L_1 + X_c)^2}}$   $I_x = 31,115 \text{ A}$

Number of poolpairs  $Pools_{motor} := 2$

frequency of varied rotation  $n_{sync} := \frac{f_v \cdot 2 \cdot \pi}{Pools_{motor}}$   $n_{sync} = 1500 \text{ rpm}$

$$n_{sha} := 1425 \text{ rpm}$$

synchron speed  $n_{syn} := 1500 \text{ rpm}$

slip  $s_1 := \frac{n_{syn} - n_{sha}}{n_{sha}} \cdot 100 \%$   $s_1 = 5,2632 \%$

$$T_{\text{motor}} := \frac{\frac{U_{\text{rms}}}{\sqrt{R_{\text{winding}}^2 + (2 \cdot \pi \cdot f_v \cdot L_1 + X_c)^2}} \cdot U_{\text{rms}}}{n_{\text{sync}}}$$

$$T_{\text{motor}} = 79,2336 \text{ N m}$$

$$P_{\text{motor}} := \frac{\frac{U_{\text{rms}}}{\sqrt{R_{\text{winding}}^2 + (2 \cdot \pi \cdot f_v \cdot L_1 + X_c)^2}} \cdot U_{\text{rms}}}{1}$$

$$P_{\text{motor}} = 12,446 \text{ kW}$$

Maximum Current over the motor on the plate

$$P_{\text{max50Hz}} := 15 \text{ kW}$$

$$I_{\text{nom}} := \frac{P_{\text{max50Hz}}}{U_{\text{rms}} \cdot \sqrt{3} \cdot 0,86 \cdot 0,95}$$

$$I_{\text{nom}} = 26,5002 \text{ A}$$